

REGISTER TRANSFER AND MICROOPERATIONS

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**
- **Arithmetic Logic Shift Unit**

REGISTER TRANSFER LANGUAGE

- Rather than specifying a digital system in words, a specific notation is used, , *register transfer language*
- For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations
- Register transfer language
 - A symbolic language
 - A convenient tool for describing the internal organization of digital computers
 - Can also be used to facilitate the design process of digital systems.

REGISTER TRANSFER

- ▣ A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action


BASIC SYMBOLS FOR REGISTER TRANSFERS

Symbols	Description	Examples
Capital letters & numerals	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow ←	Denotes transfer of information	R2 ← R1
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	A ← B, B ← A


BUS AND BUS TRANSFER

Bus is a path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations.

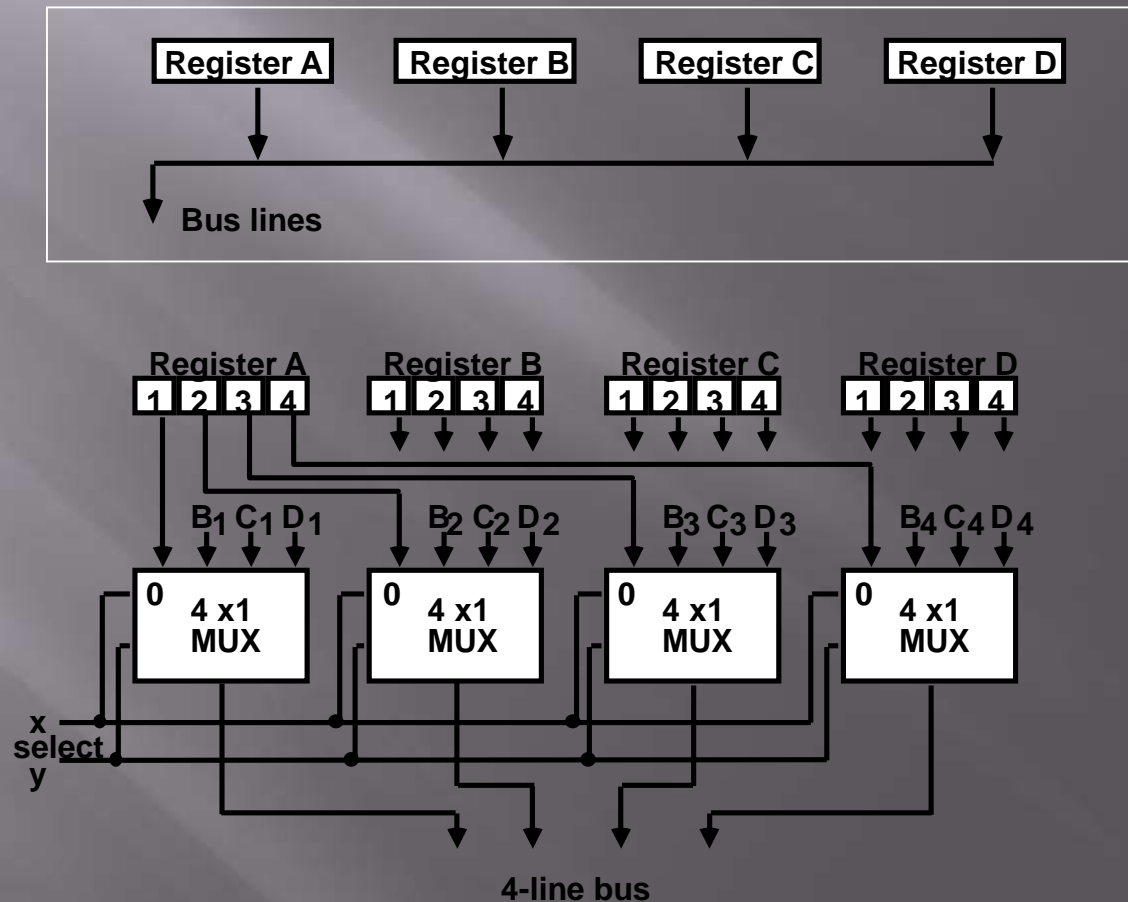From a register to bus: $BUS \leftarrow R$



 TRANSFER FROM BUS TO A DESTINATION REGISTER




Three-State Bus Buffers

Normal input A
Control input C



Output Y=A if C=1
High-impedance if C=0

Bus line with three-state buffers

 

BUS TRANSFER IN RTL

- ▣ Depending on whether the bus is to be mentioned explicitly or not, register transfer can be indicated as either


or $R2 \leftarrow R1$

$BUS \leftarrow R1, R2 \leftarrow BUS$

- ▣ In the former case the bus is implicit, but in the latter, it is explicitly indicated

MEMORY TRANSFER

- ❑ Collectively, the memory is viewed at the register level as a device, M.
- ❑ Since it contains multiple locations, we must specify which address in memory we will be using
- ❑ This is done by indexing memory references
- ❑ Memory is usually accessed in computer systems by putting the desired address in a special register, the *Memory Address Register (MAR, or AR)*
- ❑ When memory is accessed, the contents of the MAR get sent to the memory unit's address lines

 

MICROOPERATIONS

- **Arithmetic microoperations**
- **Logic microoperations**
- **Shift microoperations**

ARITHMETIC MICROOPERATIONS

- The basic arithmetic microoperations are
 - Addition
 - Subtraction
 - Increment
 - Decrement


- The additional arithmetic microoperations are
 - Add with carry
 - Subtract with borrow
 - Transfer/Load
 - etc. ...

Summary of Typical Arithmetic Micro-Operations


$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

BINARY ADDER / SUBTRACTOR / INCREMENTER


Binary Adder

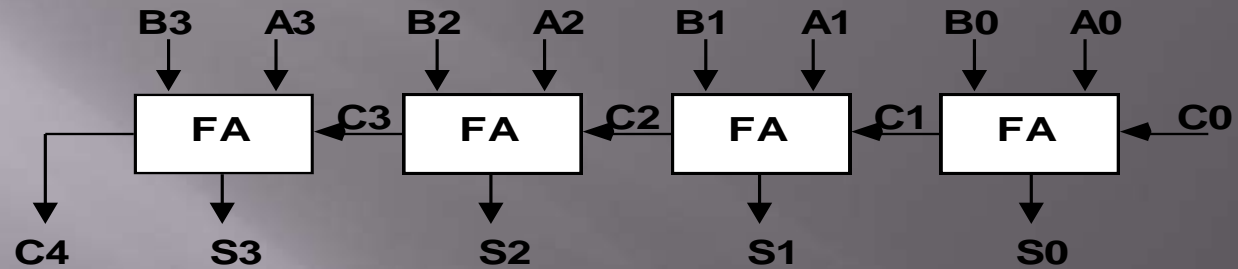


Binary Adder-Subtractor

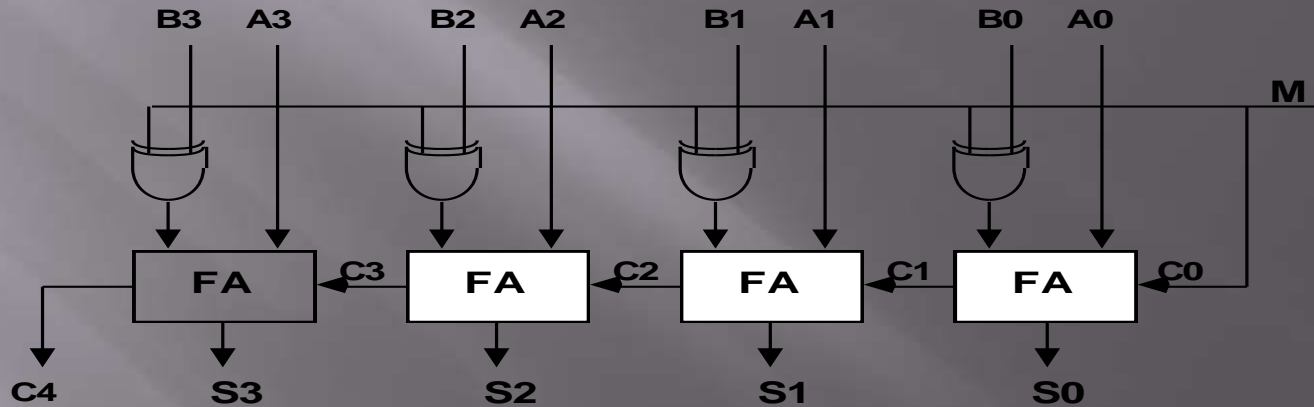

Binary Incrementer

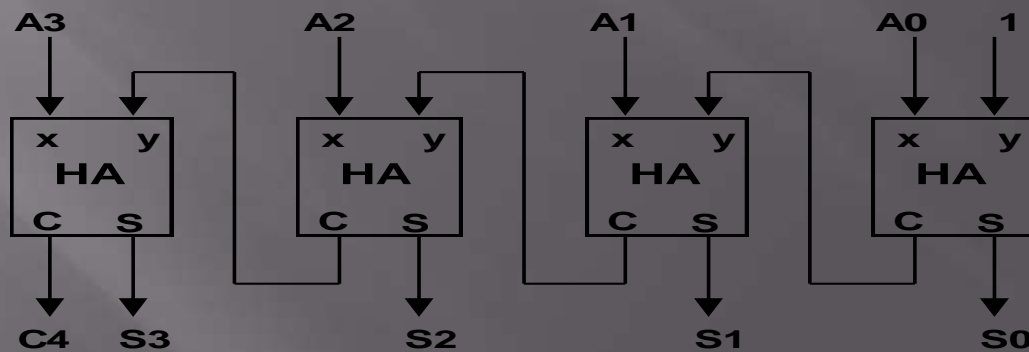

ARITHMETIC CIRCUIT

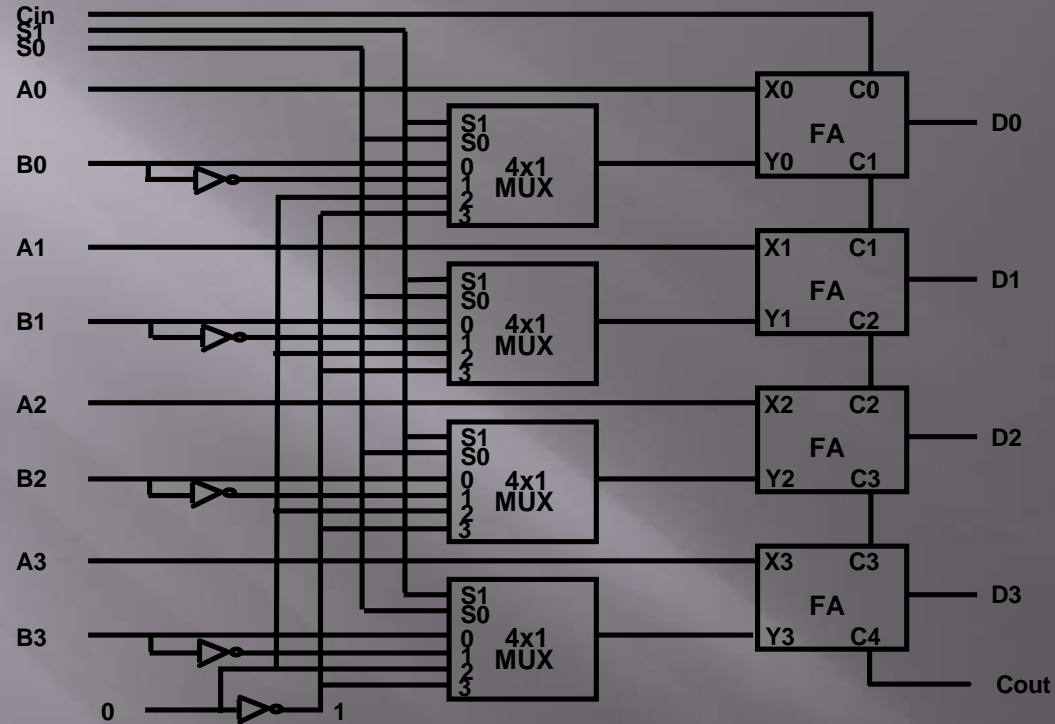

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

LOGIC MICROOPERATIONS

- Specify binary operations on the strings of bits in registers
 - Logic microoperations are bit-wise operations, i.e., they work on the individual bits of data
 - useful for bit manipulations on binary data
 - useful for making logical decisions based on the bit value
- There are, in principle, 16 different logic functions that can be defined over two binary input variables

A	B	F ₀	F ₁	F ₂	...	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	...	1	1	1
0	1	0	0	0	...	1	1	1
1	0	0	0	1	...	0	1	1
1	1	0	1	0	...	1	0	1

- However, most systems only implement four of these
 - AND (\wedge), OR (\vee), XOR (\oplus), Complement/NOT
- The others can be created from combination of these

LIST OF LOGIC MICROOPERATIONS

- List of Logic Microoperations
 - 16 different logic operations with 2 binary vars.
 - n binary vars $\rightarrow 2^{2^n}$ functions
- Truth tables for 16 functions of 2 variables and the corresponding 16 logic micro-operations

x	0 0 1 1	<i>Boolean Function</i>	<i>Micro-Operations</i>	<i>Name</i>
y	0 1 0 1			
	0 0 0 0	$F_0 = 0$	$F \leftarrow 0$	Clear
	0 0 0 1	$F_1 = xy$	$F \leftarrow A \wedge B$	AND
	0 0 1 0	$F_2 = xy'$	$F \leftarrow A \wedge B'$	
	0 0 1 1	$F_3 = x$	$F \leftarrow A$	Transfer A
	0 1 0 0	$F_4 = x'y$	$F \leftarrow A' \wedge B$	
	0 1 0 1	$F_5 = y$	$F \leftarrow B$	Transfer B
	0 1 1 0	$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
	0 1 1 1	$F_7 = x + y$	$F \leftarrow A \vee B$	OR
	1 0 0 0	$F_8 = (x + y)'$	$F \leftarrow (A \vee B)'$	NOR
	1 0 0 1	$F_9 = (x \oplus y)'$	$F \leftarrow (A \oplus B)'$	Exclusive-NOR
	1 0 1 0	$F_{10} = y'$	$F \leftarrow B'$	Complement B
	1 0 1 1	$F_{11} = x + y'$	$F \leftarrow A \vee B$	
	1 1 0 0	$F_{12} = x'$	$F \leftarrow A'$	Complement A
	1 1 0 1	$F_{13} = x' + y$	$F \leftarrow A' \vee B$	
	1 1 1 0	$F_{14} = (xy)'$	$F \leftarrow (A \wedge B)'$	NAND
	1 1 1 1	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's


APPLICATIONS OF LOGIC MICROOPERATIONS

- ▣ Logic microoperations can be used to manipulate individual bits or a portions of a word in a register

- ▣ Consider the data in a register A. In another register, B, is bit data that will be used to modify the contents of A
 - Selective-set $A \leftarrow A + B$
 - Selective-complement $A \leftarrow A \oplus B$
 - Selective-clear $A \leftarrow A \cdot B'$
 - Mask (Delete) $A \leftarrow A \cdot B$
 - Clear $A \leftarrow A \oplus B$
 - Insert $A \leftarrow (A \cdot B) + C$
 - Compare $A \leftarrow A \oplus B$
 - ...

LOGICAL SHIFT

 - ▣ In a logical shift the serial input to the shift is a 0.
- ▣ A right logical shift operation:



- ▣ A left logical shift operation:




- ▣ In a Register Transfer Language, the following notation is used
 - *shl* for a logical shift left
 - *shr* for a logical shift right
 - Examples:
 - ▣ $R2 \leftarrow shr R2$
 - ▣ $R3 \leftarrow shl R3$


CIRCULAR SHIFT

- In a circular shift the serial input is the bit that is shifted out of the other end of the register.

- A right circular shift operation:

 

- A left circular shift operation:

 


- In a RTL, the following notation is used


- *cil* for a circular shift left
- *cir* for a circular shift right
- Examples:
 - $R2 \leftarrow cir R2$
 - $R3 \leftarrow cil R3$

Logical versus Arithmetic Shift

 - ▣ A logical shift fills the newly created bit position with zero:




 - An arithmetic shift fills the newly created bit position with a copy of the number's sign bit:




ARITHMETIC SHIFT

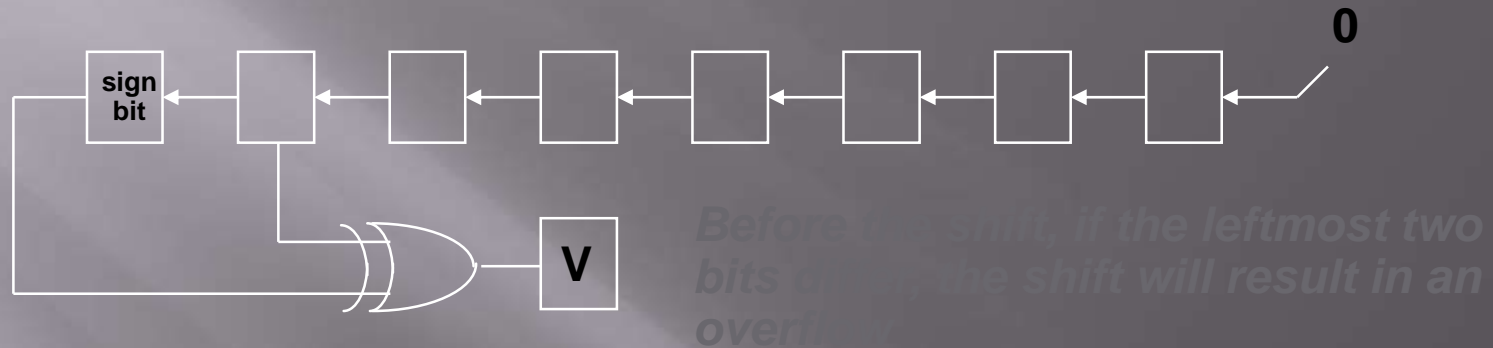- ▣ An left arithmetic shift operation must be checked for the overflow



- In a RTL, the following notation is used
 - *ashl* for an arithmetic shift left
 - *ashr* for an arithmetic shift right
 - Examples:
 - » $R2 \leftarrow ashr R2$
 - » $R3 \leftarrow ashl R3$

ARITHMETIC LOGIC SHIFT UNIT

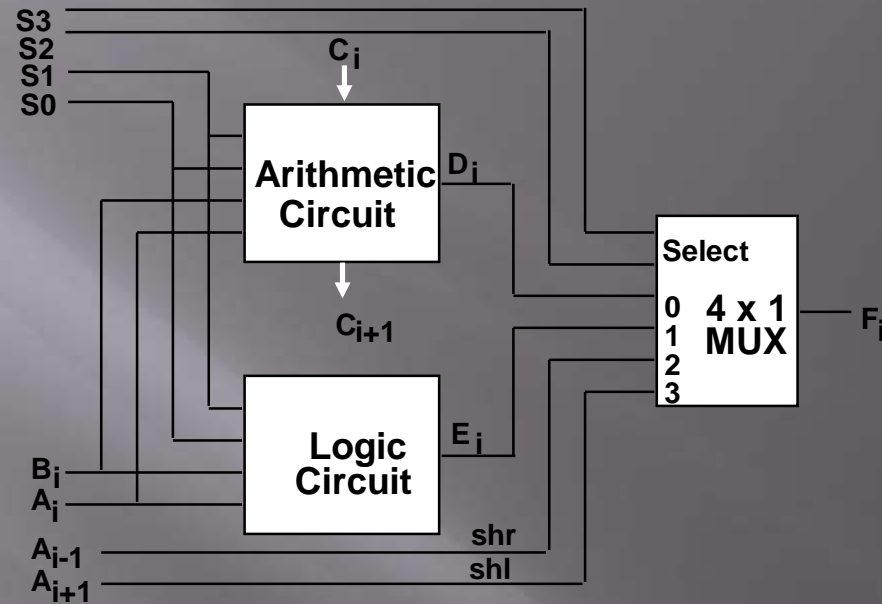

S3	S2	S1	S0	Cin	Operation	Function
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement A
1	0	X	X	X	$F = \text{shr } A$	Shift right A into F
1	1	X	X	X	$F = \text{shl } A$	Shift left A into F

CONTROL UNIT

A control unit is a major component of the computer it controls the flow of data between the CPU , memory and peripherals.

- Two major types of Control Unit
 - Hardwired Control :
 - The control logic is implemented with gates, F/Fs, decoders, and other digital circuits
 - + Fast operation, - Wiring change(if the design has to be modified)
 - Microprogrammed Control :
 - The control information is stored in a control memory, and the control memory is programmed to initiate the required sequence of microoperations
 - + Any required change can be done by updating the microprogram in control memory,

MICROPROGRAMMED CONTROL UNIT(MCU)


- Control Word

- The control variables at any given time can be represented by a string of 1's and 0's

Control Memory

- A memory is part of a control unit : *Microprogram*
- Computer Memory (*employs a microprogrammed control unit*)
 - Main Memory : for storing user program (*Machine instruction/data*)
 - Control Memory : for storing microprogram (*Microinstruction*)

Microprogrammed Control Organization

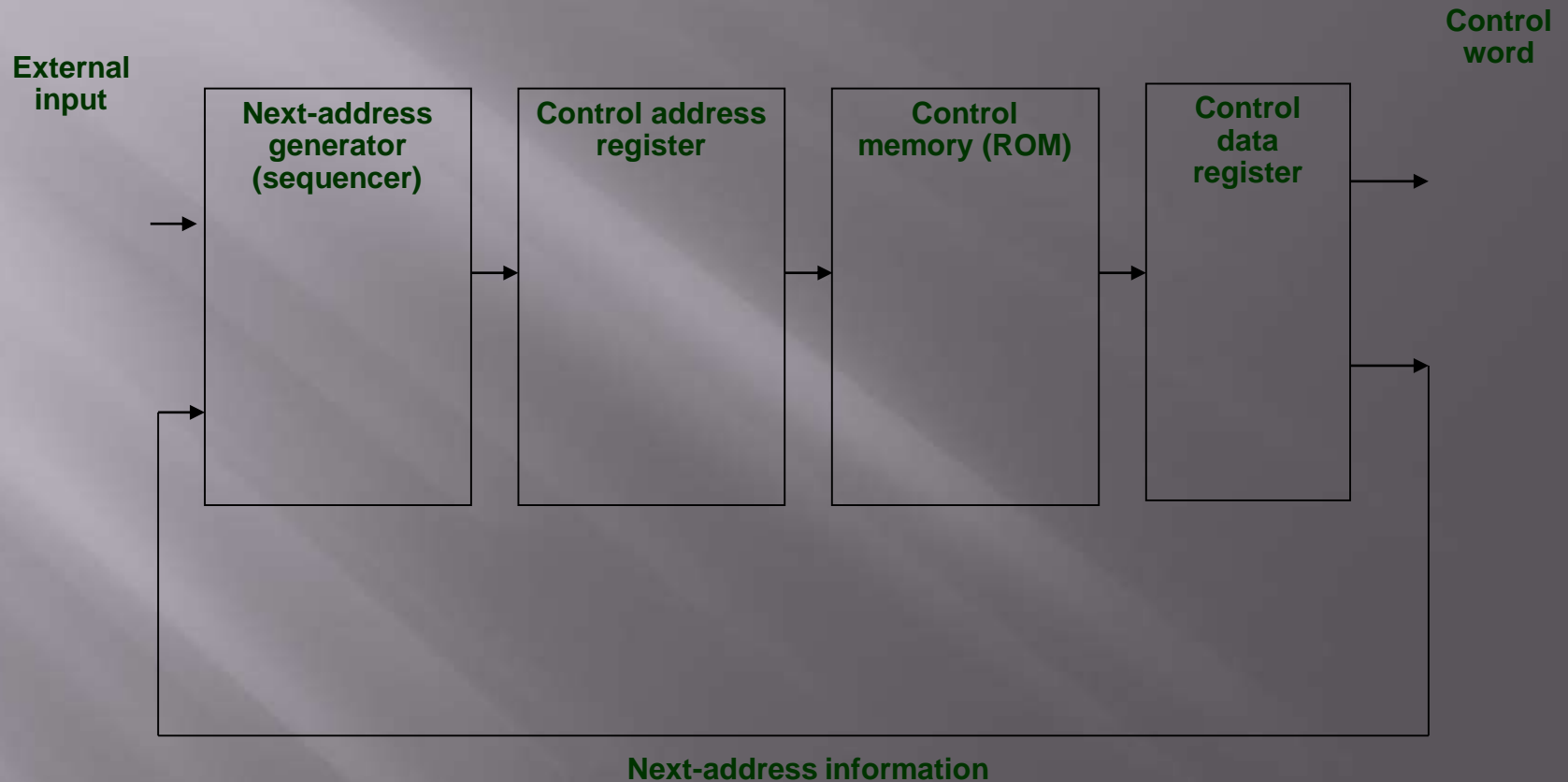

INPUT-OUTPUT ORGANIZATION

- ▣ INPUT-OUTPUT ORGANIZATION

- ▣ Provides a method for transferring information between internal storage (such as memory and CPU registers) and external I/O devices

- ▣ Resolves the *differences* between the computer and peripheral devices
 - Peripherals - Electromechanical Devices
 - CPU or Memory - Electronic Device


I/O BUS AND INTERFACE MODULES

- ▣ Each peripheral has an interface module associated with it

Interface

- ▣ - Decodes the device address (device code)
- ▣ - Decodes the commands (operation)
- ▣ - Provides signals for the peripheral controller
- ▣ - Synchronizes the data flow and supervises
- ▣ the transfer rate between peripheral and CPU or Memory

I/O BUS AND INTERFACE MODULES

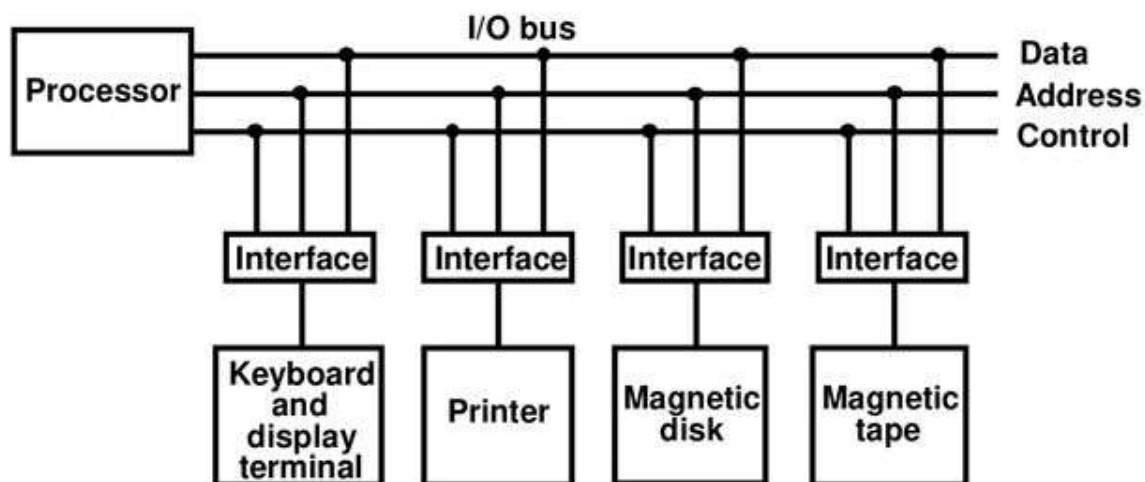


Each peripheral has an interface module associated with it

Interface

- Decodes the device address (device code)
- Decodes the commands (operation)
- Provides signals for the peripheral controller
- Synchronizes the data flow and supervises the transfer rate between peripheral and CPU or Memory

Typical I/O instruction

 


I/O BUS AND MEMORY BUS

▣ Functions of Buses

- *MEMORY BUS* is for information transfers between CPU and the MM
- * *I/O BUS* is for information transfers between CPU and I/O devices through their I/O interface

I/O INTERFACE

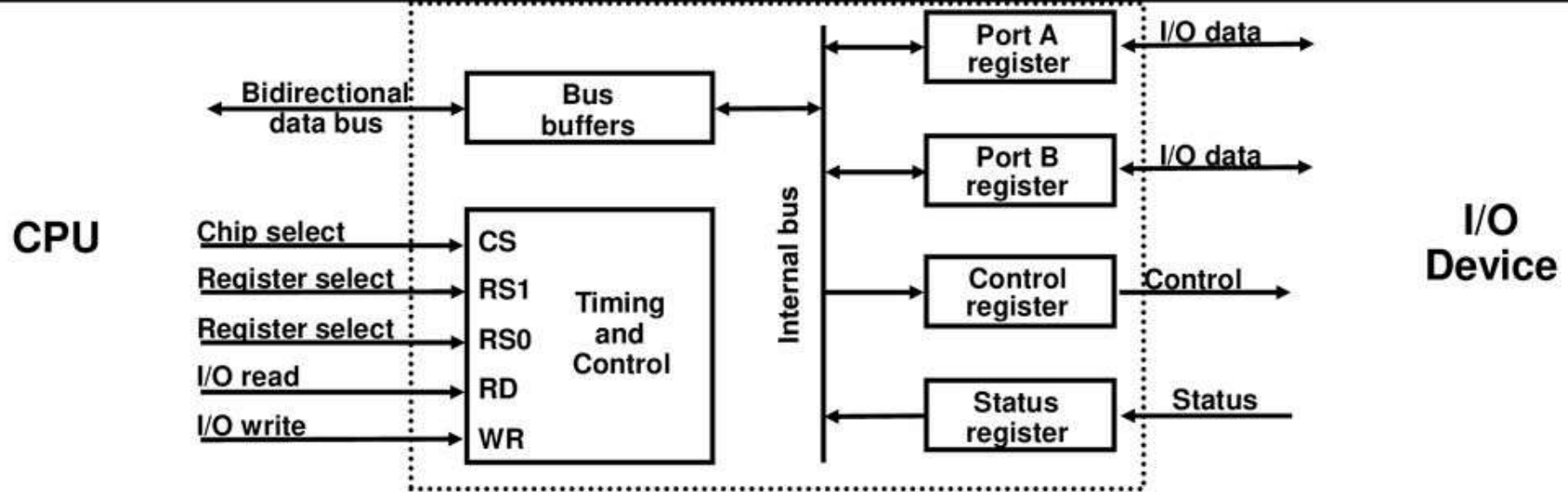

CS	RS1	RS0	Register selected
0	x	x	None - data bus in high-impedance
1	0	0	Port A register
1	0	1	Port B register
1	1	0	Control register
1	1	1	Status register

Programmable Interface



- Information in each port can be assigned a meaning depending on the mode of operation of the I/O device
 - Port A = Data; Port B = Command; Port C = Status
- CPU initializes(loads) each port by transferring a byte to the Control Register
 - Allows CPU can define the mode of operation of each port
 - *Programmable Port*: By changing the bits in the control register, it is possible to change the interface characteristics

Strobe Control

- Employs a single control line to time each transfer
- The strobe may be activated by either the source or the destination unit


Source-Initiated Strobe for Data Transfer

Block Diagram

  

Destination-Initiated Strobe for Data Transfer

Block Diagram

 

Timing Diagram



HANDSHAKING

▣ Strobe Methods

Source-Initiated

The source unit that initiates the transfer has no way of knowing whether the destination unit has actually received data


▣ Destination-Initiated

The destination unit that initiates the transfer has no way of knowing whether the source has actually placed the data on the bus


To solve this problem, the *HANDSHAKE* method introduces a second control signal to provide a *Reply* to the unit that initiates the transfer

SOURCE-INITIATED TRANSFER USING HANDSHAKE


Block Diagram

 

Timing Diagram

 


Sequence of Events

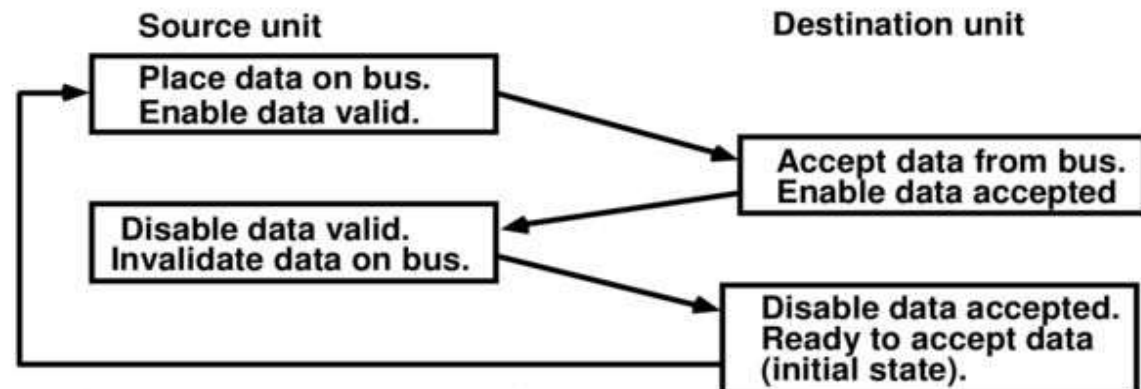


- * Allows arbitrary delays from one state to the next
- * Permits each unit to respond at its own data transfer rate
- * The rate of transfer is determined by the slower unit

Destination initiated transfer

Block Diagram

 

Timing Diagram

 

Sequence of Events

